

سوال (۱)

در تشخیص زوج یا فرد بودن تعداد یک‌ها، آمدم پرارزش‌ترین بیت را با بیت کناری XOR کردیم و نتیجه را با بیت بعدی، به XOR کردن ادامه دادیم. اگر خروجی یک می‌شد یعنی تعداد یک‌ها فرد است و اگر صفر می‌شد، یعنی تعداد زوج است.

کد ماژول:

```
library IEEE;
```

```
USE ieee.std_logic_1164.all ;
```

```
USE ieee.std_logic_unsigned.all ;
```

```
use IEEE.NUMERIC_STD.ALL;
```

```
entity evenodd is
```

```
Port (a:in STD_LOGIC_VECTOR (7 downto 0);
```

```
b: out STD_LOGIC_VECTOR (7 downto 0));
```

```
end evenodd;
```

```
architecture Behavioral of evenodd is
```

```
signal q: std_logic;
```

```
signal y, z, w, s, two: std_logic_vector(7 downto 0);
```

```

begin

q <=(((((((((a(7) xor a(6))xor a(5))xor a(4))xor a(3))xor a(2))xor a(1))xor
a(0))));

y <= a + x"2F";

z <= a-x"25";

w <= (y(0)&y(7)&y(6)&y(5)&y(4)&y(3)&y(2)&y(1));

s <= (z(6)&z(5)&z(4)&z(3)&z(2)&z(1)&z(0)&z(7));

with q select

b <= (s) when ('1'),

(w) when ('0'),

(x"00") when others;

end Behavioral;

```

برای ضرب در ۲ یا تقسیم بر ۲ کردن از شیفت دادن بیت‌ها استفاده کردیم.

کد تست‌بنچ:

```

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.NUMERIC_STD.ALL;

```

entity evenodd_tb is

end evenodd_tb;

architecture Behavioral of evenodd_tb is

component evenodd

PORT(

a: in std_logic_vector(7 downto 0);

b: out STD_LOGIC_VECTOR (8 downto 0)

);

end component;

signal a: std_logic_vector(7 downto 0):= (others => '0');

signal b: std_logic_vector(7 downto 0):= (others => '0');

begin

process

begin

a <= x"4B";

wait for 2 ps;

a <= x"7A";


```
wait;
```

```
end process;
```

```
U: entity work.evenodd(behavioral) PORT MAP(a=>a, b=>b);
```

```
end Behavioral;
```

نتیجه شبیه‌سازی:

 

این یک شبیه‌سازی محدود بوده و اگر می‌خواستیم تمامی جوانب این سوال را بررسی کنیم، باید محاسبات floating point یا اعشاری نیز انجام می‌دادیم. از عملکرد تقسیم نمی‌توانستیم استفاده کنیم زیرا قابل سنتز نیست.

در صورت سرریز کردن می‌توانستیم بیت پورت `b` را بیش‌تر کنیم.

بخش‌های مورد نظر گزارش سنتز:

Detailed RTL Component Info :

----Adders :

2 Input 8 Bit Adders := 2

----XORs :

8 Input 1 Bit XORs := 1

----Muxes :

2 Input 8 Bit Muxes := 1

| Site Type | Used | Fixed | Prohibited | Available | Util% |
|-----------------------|------|-------|------------|-----------|-------|
| Slice LUTs* | 15 | 0 | 0 | 303600 | <0.01 |
| LUT as Logic | 15 | 0 | 0 | 303600 | <0.01 |
| LUT as Memory | 0 | 0 | 0 | 130800 | 0.00 |
| Slice Registers | 0 | 0 | 0 | 607200 | 0.00 |
| Register as Flip Flop | 0 | 0 | 0 | 607200 | 0.00 |
| Register as Latch | 0 | 0 | 0 | 607200 | 0.00 |
| F7 Muxes | 0 | 0 | 0 | 151800 | 0.00 |
| F8 Muxes | 0 | 0 | 0 | 75900 | 0.00 |


2. Memory

| Site Type | Used | Fixed | Prohibited | Available | Util% |
|----------------|------|-------|------------|-----------|-------|
| Block RAM Tile | 0 | 0 | 0 | 1030 | 0.00 |
| RAMB36/FIFO* | 0 | 0 | 0 | 1030 | 0.00 |
| RAMB18 | 0 | 0 | 0 | 2060 | 0.00 |

3. DSP

| Site Type | Used | Fixed | Prohibited | Available | Util% |
|-----------|------|-------|------------|-----------|-------|
| DSPs | 0 | 0 | 0 | 2800 | 0.00 |

| Site Type | Used | Fixed | Prohibited | Available | Util% |
|-----------------------------|------|-------|------------|-----------|-------|
| Bonded IOB | 16 | 0 | 0 | 600 | 2.67 |
| Bonded IPADs | 0 | 0 | 0 | 62 | 0.00 |
| Bonded OPADs | 0 | 0 | 0 | 40 | 0.00 |
| PHY_CONTROL | 0 | 0 | 0 | 14 | 0.00 |
| PHASER_REF | 0 | 0 | 0 | 14 | 0.00 |
| OUT_FIFO | 0 | 0 | 0 | 56 | 0.00 |
| IN_FIFO | 0 | 0 | 0 | 56 | 0.00 |
| IDELAYCTRL | 0 | 0 | 0 | 14 | 0.00 |
| IBUFDS | 0 | 0 | 0 | 576 | 0.00 |
| GTXE2_COMMON | 0 | 0 | 0 | 5 | 0.00 |
| GTXE2_CHANNEL | 0 | 0 | 0 | 20 | 0.00 |
| PHASER_OUT/PHASER_OUT_PHY | 0 | 0 | 0 | 56 | 0.00 |
| PHASER_IN/PHASER_IN_PHY | 0 | 0 | 0 | 56 | 0.00 |
| IDELAYE2/IDELAYE2_FINEDELAY | 0 | 0 | 0 | 700 | 0.00 |
| ODELAYE2/ODELAYE2_FINEDELAY | 0 | 0 | 0 | 700 | 0.00 |
| IBUFDS_GTE2 | 0 | 0 | 0 | 10 | 0.00 |
| ILOGIC | 0 | 0 | 0 | 600 | 0.00 |
| OLOGIC | 0 | 0 | 0 | 600 | 0.00 |

 

سوال دوم)

طراحی stopwatch

کد اصلی ماژول:

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use ieee.std_logic_unsigned.all;
```

entity stopwatch is

```
Port (  
    clk    : in STD_LOGIC;  
    rst    : in STD_LOGIC;  
    start  : in STD_LOGIC;  
    sec_100 : out STD_LOGIC_VECTOR (7 downto 0);  
    sec    : out STD_LOGIC_VECTOR (7 downto 0);  
    min    : out STD_LOGIC_VECTOR (7 downto 0)  
);
```

end stopwatch;

architecture Behavioral of stopwatch is

```
signal s_100 : STD_LOGIC_VECTOR (7 downto 0) := (others => '0');  
signal s    : STD_LOGIC_VECTOR (7 downto 0) := (others => '0');  
signal m    : STD_LOGIC_VECTOR (7 downto 0) := (others => '0');
```

begin

process(clk, rst)

begin

if rst = '1' then

s_100 <= (others => '0');

```
s    <= (others => '0');  
m    <= (others => '0');  
elsif rising_edge(clk) then  
    if start = '1' then  
        s_100 <= s_100 + 1;  
        if s_100 = 99 then  
            s_100 <= (others => '0');  
            s <= s + 1;  
            if s = 59 then  
                s <= (others => '0');  
                m <= m + 1;  
                if m = 59 then  
                    m <= (others => '0');  
                end if;  
            end if;  
        end if;  
    end if;  
end if;  
end process;
```



```
sec_100 <= s_100;
```

```
sec    <= s;
```

```
min    <= m;
```

```
end Behavioral;
```

کد تست بنچ:

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
use IEEE.NUMERIC_STD.ALL;
```

```
use ieee.std_logic_arith.all;
```

```
use ieee.std_logic_unsigned.all;
```

```
entity stopwatch_tb is
```

```
end stopwatch_tb;
```

```
architecture Behavioral of stopwatch_tb is
```

```
component stopwatch
```

```
    Port ( clk : in STD_LOGIC;
```

```
          rst : in STD_LOGIC;
```

```
          start : in STD_LOGIC;
```

```

        sec_100 : out STD_LOGIC_VECTOR (7 downto 0);

        sec : out STD_LOGIC_VECTOR (7 downto 0);

        min : out STD_LOGIC_VECTOR (7 downto 0));

end component;

signal clk :STD_LOGIC:= '0';

signal rst, start :STD_LOGIC:= '0';

signal sec_100: std_logic_vector(7 downto 0);


signal sec: std_logic_vector(7 downto 0);
signal min: std_logic_vector(7 downto 0);


constant CLK_PERIOD : time := 2 ps;

begin


    -- Clock generation

    clk <= not clk after CLK_PERIOD/2;


process

begin

```




```
rst <= '1';  
wait for 4 ps;  
rst <= '0';  
start <= '1';  
wait for 50000 ps;  
rst <='1';  
start <= '0';
```


```
wait;  
end process;
```

```
U: entity work.stopwatch(behavioral) PORT MAP( clk=>clk,  
    rst =>rst,  
    start => start,  
    sec_100 => sec_100,  
    sec => sec,  
    min => min);
```

```
end Behavioral;
```

نتایج شبیه‌سازی:

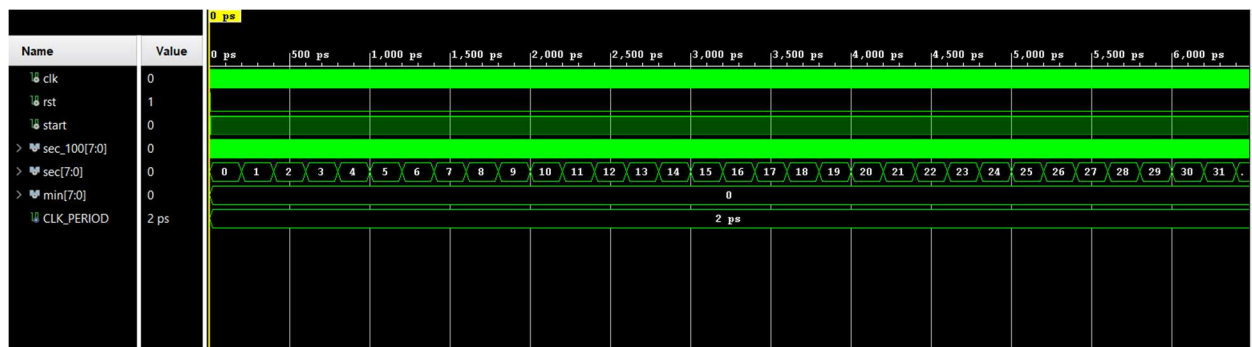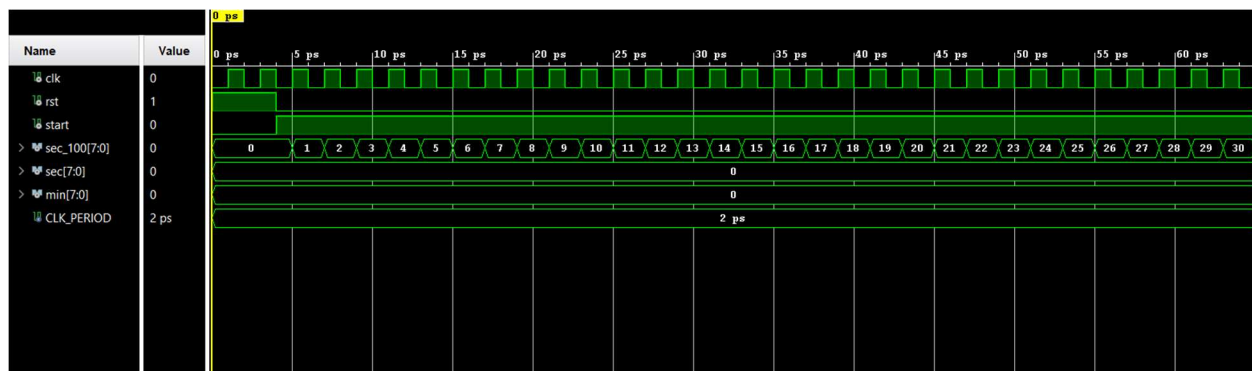 

 

نتایج مورد نظر سنتز:

Detailed RTL Component Info :

+---Adders :

2 Input 8 Bit Adders := 3

+---Registers :

8 Bit Registers := 3

+---Muxes :

2 Input 8 Bit Muxes := 3

| Site Type | Used | Fixed | Prohibited | Available | Util% |
|-----------------------|------|-------|------------|-----------|-------|
| Slice LUTs* | 30 | 0 | 0 | 303600 | <0.01 |
| LUT as Logic | 30 | 0 | 0 | 303600 | <0.01 |
| LUT as Memory | 0 | 0 | 0 | 130800 | 0.00 |
| Slice Registers | 24 | 0 | 0 | 607200 | <0.01 |
| Register as Flip Flop | 24 | 0 | 0 | 607200 | <0.01 |
| Register as Latch | 0 | 0 | 0 | 607200 | 0.00 |
| F7 Muxes | 0 | 0 | 0 | 151800 | 0.00 |
| F8 Muxes | 0 | 0 | 0 | 75900 | 0.00 |

2. Memory


| Site Type | Used | Fixed | Prohibited | Available | Util% |
|----------------|------|-------|------------|-----------|-------|
| Block RAM Tile | 0 | 0 | 0 | 1030 | 0.00 |
| RAMB36/FIFO* | 0 | 0 | 0 | 1030 | 0.00 |
| RAMB18 | 0 | 0 | 0 | 2060 | 0.00 |

| Site Type | Used | Fixed | Prohibited | Available | Util% |
|-----------------------------|------|-------|------------|-----------|-------|
| Bonded IOB | 27 | 0 | 0 | 600 | 4.50 |
| Bonded IPADs | 0 | 0 | 0 | 62 | 0.00 |
| Bonded OPADs | 0 | 0 | 0 | 40 | 0.00 |
| PHY_CONTROL | 0 | 0 | 0 | 14 | 0.00 |
| PHASER_REF | 0 | 0 | 0 | 14 | 0.00 |
| OUT_FIFO | 0 | 0 | 0 | 56 | 0.00 |
| IN_FIFO | 0 | 0 | 0 | 56 | 0.00 |
| IDELAYCTRL | 0 | 0 | 0 | 14 | 0.00 |
| IBUFDS | 0 | 0 | 0 | 576 | 0.00 |
| GTXE2_COMMON | 0 | 0 | 0 | 5 | 0.00 |
| GTXE2_CHANNEL | 0 | 0 | 0 | 20 | 0.00 |
| PHASER_OUT/PHASER_OUT_PHY | 0 | 0 | 0 | 56 | 0.00 |
| PHASER_IN/PHASER_IN_PHY | 0 | 0 | 0 | 56 | 0.00 |
| IDELAYE2/IDELAYE2_FINEDELAY | 0 | 0 | 0 | 700 | 0.00 |
| ODELAYE2/ODELAYE2_FINEDELAY | 0 | 0 | 0 | 700 | 0.00 |
| IBUFDS_GTE2 | 0 | 0 | 0 | 10 | 0.00 |
| ILOGIC | 0 | 0 | 0 | 600 | 0.00 |
| OLOGIC | 0 | 0 | 0 | 600 | 0.00 |

5. Clocking

| Site Type | Used | Fixed | Prohibited | Available | Util% |
|------------|------|-------|------------|-----------|-------|
| BUFGCTRL | 1 | 0 | 0 | 32 | 3.13 |
| BUFIO | 0 | 0 | 0 | 56 | 0.00 |
| MMCME2_ADV | 0 | 0 | 0 | 14 | 0.00 |
| PLLE2_ADV | 0 | 0 | 0 | 14 | 0.00 |
| BUFMRCE | 0 | 0 | 0 | 28 | 0.00 |
| BUFHCE | 0 | 0 | 0 | 168 | 0.00 |
| BUFR | 0 | 0 | 0 | 56 | 0.00 |

| Ref Name | Used | Functional Category |
|----------|------|---------------------|
| OBUF | 24 | IO |
| FDCE | 24 | Flop & Latch |
| LUT6 | 19 | LUT |
| LUT4 | 5 | LUT |
| LUT2 | 5 | LUT |
| LUT5 | 4 | LUT |
| LUT3 | 3 | LUT |
| IBUF | 3 | IO |
| LUT1 | 2 | LUT |
| BUFG | 1 | Clock |

 

سوال سوم)

تقسیم‌کننده فرکانسی با duty cycle مشخص

(پورت‌های خروجی tenc و count برای کنترل شمارش است و می‌توانسیم کلاً آن‌ها را حذف کنیم و تنها به‌عنوان سیگنال داشته باشیم.)

کد اصلی ماژول:

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.std_logic_unsigned.all;

use IEEE.std_logic_arith.all;

--use IEEE.NUMERIC_STD.ALL;
```

entity duty is

```
Port ( clk : in STD_LOGIC;

      c : in STD_LOGIC_VECTOR (3 downto 0);
```

```
    wave : out STD_LOGIC;  
    count, tenc : out STD_LOGIC_VECTOR (7 downto 0));  
end duty;
```

architecture Behavioral of duty is

```
signal cc, b, ten : std_logic_vector (7 downto 0) := x"00";
```

```
signal ww : std_logic := '0';
```

```
begin
```

```
process(clk)
```

```
begin
```

```
if clk='0' then
```

```
    if ten /=99 then
```

```
        if c/=0 then
```

```
            if cc/=((c)*x"A") then
```

```
                cc <= cc+'1';
```

```
            if c/=0 then
```

```
                ww <= '1';
```

```
            else
```

```
                ww<='0';
```



```
        end if;

    else

        ww <= '0';

    end if;

    else

        ww <= '0';

    end if;

    ten <= ten +'1';

    else

        ten <= x"00";

        cc <= x"00";

    end if;

end if;

end process;

count <= cc;

wave <= ww;

tenc <= ten;

end Behavioral;
```

```
library IEEE;
```

کد تست پنج:

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
use IEEE.NUMERIC_STD.ALL;
```

```
use ieee.std_logic_arith.all;
```

```
use ieee.std_logic_unsigned.all;
```

```
entity duty_tb is
```

```
end duty_tb;
```

```
architecture Behavioral of duty_tb is
```

```
component duty
```

```
    Port ( clk : in STD_LOGIC;
```

```
          c : in STD_LOGIC_VECTOR (3 downto 0);
```

```
          wave : out STD_LOGIC;
```

```
          count, tenc : out STD_LOGIC_VECTOR (7 downto 0));
```

```
end component;
```

```
signal clk :STD_LOGIC:= '0';
```

```
signal wave :STD_LOGIC:= '0';
```

```
signal c: std_logic_vector(3 downto 0);
```

```
signal count, tenc : STD_LOGIC_VECTOR (7 downto 0);
```

```
constant CLK_PERIOD : time := 2 ps;
```

```
begin
```

```
    -- Clock generation
```

```
    clk <= not clk after CLK_PERIOD/2;
```

```
process
```

```
begin
```

```
c <= x"3";
```

```
wait for 400 ps;
```

```
c <= x"1";
```

```
wait for 400 ps;
```

```
c <= x"7";
```

```
wait for 400 ps;
```

```
c<= x"A";
```

```
wait;
```

```
end process;
```

U: entity work.duty(behavioral) PORT MAP(clk=>clk,

c =>c,



wave => wave,




tenc => tenc,

count => count);

end Behavioral;

نتایج شبیه‌سازی:

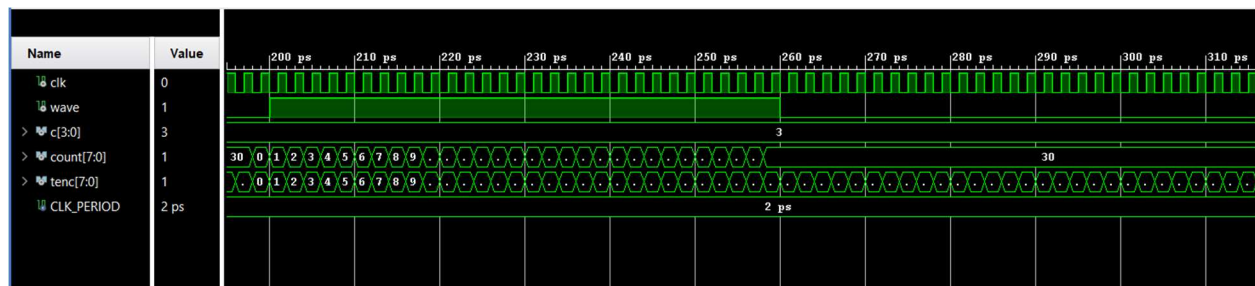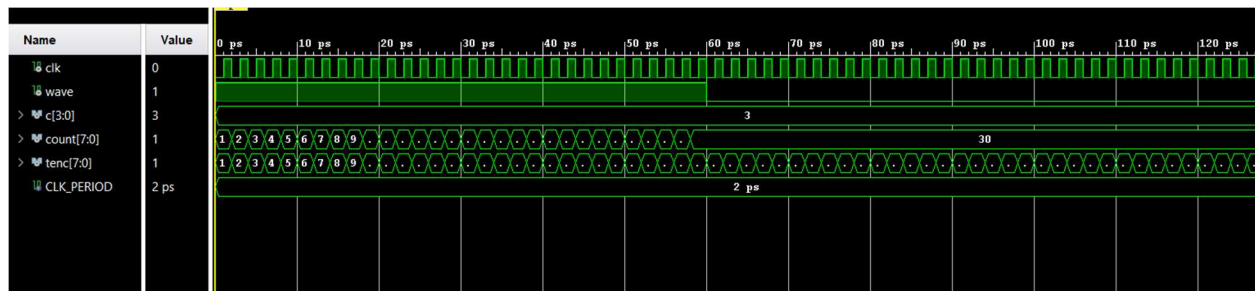

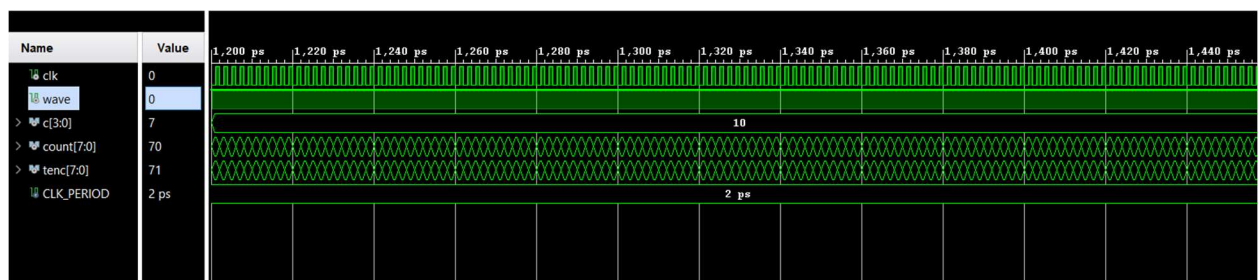 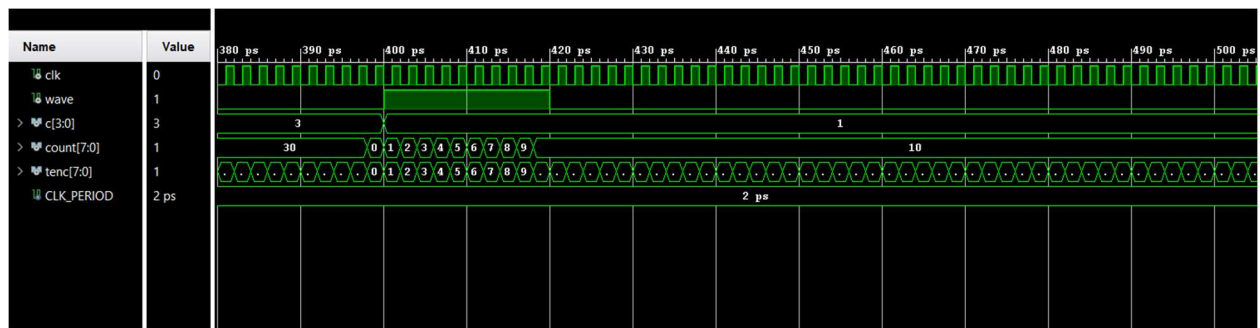

نتایج مورد نظر سنتز:

Detailed RTL Component Info :

+---Adders :

2 Input 8 Bit Adders := 2

+---Muxes :

2 Input 8 Bit Muxes := 2

2 Input 1 Bit Muxes := 1

| Site Type | Used | Fixed | Prohibited | Available | Util% |
|-----------------------|------|-------|------------|-----------|-------|
| Slice LUTs* | 21 | 0 | 0 | 303600 | <0.01 |
| LUT as Logic | 21 | 0 | 0 | 303600 | <0.01 |
| LUT as Memory | 0 | 0 | 0 | 130800 | 0.00 |
| Slice Registers | 17 | 0 | 0 | 607200 | <0.01 |
| Register as Flip Flop | 0 | 0 | 0 | 607200 | 0.00 |
| Register as Latch | 17 | 0 | 0 | 607200 | <0.01 |
| F7 Muxes | 0 | 0 | 0 | 151800 | 0.00 |
| F8 Muxes | 0 | 0 | 0 | 75900 | 0.00 |

1.1 Summary of Registers by Type

| Total | Clock Enable | Synchronous | Asynchronous |
|-------|--------------|-------------|--------------|
| 0 | - | - | - |
| 0 | - | - | Set |
| 0 | - | - | Reset |
| 0 | - | Set | - |
| 0 | - | Reset | - |
| 0 | Yes | - | - |
| 0 | Yes | - | Set |
| 17 | Yes | - | Reset |
| 0 | Yes | Set | - |
| 0 | Yes | Reset | - |

2. Memory

| Site Type | Used | Fixed | Prohibited | Available | Util% |
|----------------|------|-------|------------|-----------|-------|
| Block RAM Tile | 0 | 0 | 0 | 1030 | 0.00 |
| RAMB36/FIFO* | 0 | 0 | 0 | 1030 | 0.00 |
| RAMB18 | 0 | 0 | 0 | 2060 | 0.00 |

| Site Type | Used | Fixed | Prohibited | Available | Util% |
|-----------------------------|------|-------|------------|-----------|-------|
| Bonded IOB | 22 | 0 | 0 | 600 | 3.67 |
| Bonded IPADs | 0 | 0 | 0 | 62 | 0.00 |
| Bonded OPADs | 0 | 0 | 0 | 40 | 0.00 |
| PHY_CONTROL | 0 | 0 | 0 | 14 | 0.00 |
| PHASER_REF | 0 | 0 | 0 | 14 | 0.00 |
| OUT_FIFO | 0 | 0 | 0 | 56 | 0.00 |
| IN_FIFO | 0 | 0 | 0 | 56 | 0.00 |
| IDELAYCTRL | 0 | 0 | 0 | 14 | 0.00 |
| IBUFDS | 0 | 0 | 0 | 576 | 0.00 |
| GTXE2_COMMON | 0 | 0 | 0 | 5 | 0.00 |
| GTXE2_CHANNEL | 0 | 0 | 0 | 20 | 0.00 |
| PHASER_OUT/PHASER_OUT_PHY | 0 | 0 | 0 | 56 | 0.00 |
| PHASER_IN/PHASER_IN_PHY | 0 | 0 | 0 | 56 | 0.00 |
| IDELAYE2/IDELAYE2_FINEDELAY | 0 | 0 | 0 | 700 | 0.00 |
| ODELAYE2/ODELAYE2_FINEDELAY | 0 | 0 | 0 | 700 | 0.00 |
| IBUFDS_GTE2 | 0 | 0 | 0 | 10 | 0.00 |
| ILOGIC | 0 | 0 | 0 | 600 | 0.00 |
| OLOGIC | 0 | 0 | 0 | 600 | 0.00 |

5. Clocking

| Site Type | Used | Fixed | Prohibited | Available | Util% |
|------------|------|-------|------------|-----------|-------|
| BUFGCTRL | 1 | 0 | 0 | 32 | 3.13 |
| BUFIO | 0 | 0 | 0 | 56 | 0.00 |
| MMCME2_ADV | 0 | 0 | 0 | 14 | 0.00 |
| PLLE2_ADV | 0 | 0 | 0 | 14 | 0.00 |
| BUFMRCE | 0 | 0 | 0 | 28 | 0.00 |
| BUFHCE | 0 | 0 | 0 | 168 | 0.00 |
| BUFR | 0 | 0 | 0 | 56 | 0.00 |

7. Primitives

| Ref Name | Used | Functional Category |
|----------|------|---------------------|
| OBUF | 17 | IO |
| LDCE | 17 | Flop & Latch |
| LUT6 | 7 | LUT |
| LUT3 | 7 | LUT |
| LUT5 | 6 | LUT |
| LUT4 | 6 | LUT |
| IBUF | 5 | IO |
| LUT2 | 4 | LUT |
| BUFG | 1 | Clock |

